

*Heaven's Light is Our Guide*



# Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

## Lab Report

Course Code	<b>ECE 1202</b>
Course Title	Circuit and System-   Sessional
Date of Submission	03-09-2024

<b>Submitted By:</b>	<b>Submitted To:</b>
<b>Name : Arafat Rahman</b>	<b>Oishi Jyoti</b>
<b>Roll : 2210059</b>	<b>Lecturer</b>
<b>Registration : 1113</b>	<b>Department of Electrical and Computer Engineering</b>
<b>Session : 2022-2023</b>	<b>RUET</b>
<b>Department of ECE, RUET</b>	

**Name of The Experiment:** Study the relationship between phase and line voltages of wye connected 3-φ balanced system.

**Theory:** In a balanced three-phase system, the three-phase voltages have the same magnitude and are displaced by 120 degrees from each other. In a wye-connected three-phase balanced system, there is a specific relationship between the phase voltages and the line voltages. The phase voltage ( $V_p$ ) is the voltage between any phase and the neutral point, while the line voltage ( $V_L$ ) is the voltage between any two phases. Due to the wye-connection, where the neutral point of the three-phase system is connected to the common point, the line voltage is equal to the phase voltage multiplied by the square root of 3 ( $\sqrt{3}$ ). Mathematically, this relationship can be expressed as,

$$V_p = \frac{V_L}{\sqrt{3}}$$
$$I_p = I_L$$

**Circuit:**

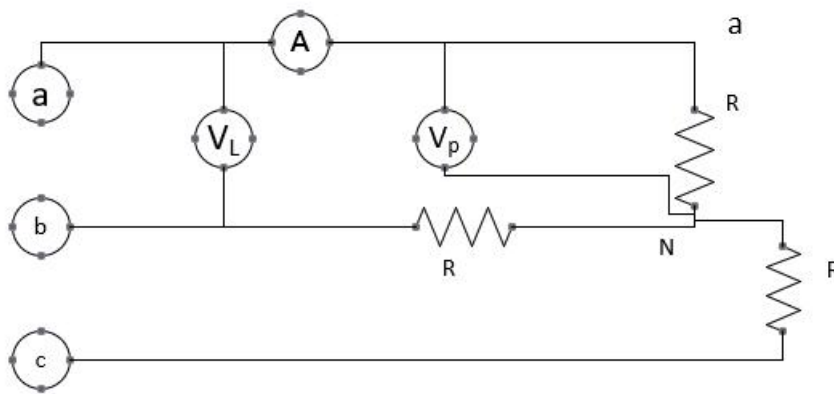


Fig. Circuit Diagram

**Required Apparatus:**

1. Source
2. Ammeter
3. Resistor
4. Multimeter
5. Connecting Wire

**Data Table:**

SL No	V <sub>L</sub>	V <sub>P(m)</sub>	V <sub>P(c)</sub>	I <sub>L</sub>	I <sub>P</sub>	Error(%)
1	74.6	44	43.07	0.37	0.37	2.114
2	92.8	54	53.59	0.49	0.49	0.76
3	39.60	23.34	22.86	0.23	0.23	2.1

**Calculation:**

For 1st calculation,

$$V_L = 74.6 \text{ V}, V_{P(c)} = V_L / \sqrt{3} = 43.07 \text{ V}, V_{P(m)} = 44 \text{ V}, \text{Error} = 2.114\%$$

For 2nd calculation,

$$V_L = 92.8 \text{ V}, V_{P(c)} = V_L / \sqrt{3} = 53.59 \text{ V}, V_{P(m)} = 54 \text{ V}, \text{Error} = 0.76\%$$

For 3rd calculation,

$$V_L = 39.60 \text{ V}, V_{P(c)} = V_L / \sqrt{3} = 22.86 \text{ V}, V_{P(m)} = 23.34 \text{ V}, \text{Error} = 2.1\%$$

**Conclusion:**

The experiment investigated the relationship between phase and line voltages in a balanced wye connected three-phase system. The results confirmed the theoretical relationship ( $V_L = \sqrt{3} * V_P$ ). This experiment demonstrates the fundamental concept of voltage relationships in a common three-phase system configuration.