

*Heaven's Light is Our Guide*



# Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering

## Lab Report

Course Code	<b>ECE 1202</b>
Course Title	Circuits and Systems II Sessional
Date of Submission	03-09-2024

<b>Submitted By:</b>	<b>Submitted To:</b>
<b>Name : Noushin Tabassum</b>	<b>Oishi Jyoti</b>
<b>Roll : 2210058</b>	<b>Assistant Professor</b>
<b>Registration : 1112</b>	<b>Department of Electrical and</b>
<b>Session : 2022-2023</b>	<b>Computer Engineering</b>
<b>Department of ECE, RUET</b>	<b>RUET</b>

**Name of the Experiment:** Study the relation between line current and phase current of a delta connected 3 phase balanced system.

**Theory:** In a balanced three-phase system, the three-phase voltages have the same magnitude and are displaced by 120 degrees from each other. In a delta-connected system, Phase Current ( $I_P$ ) is the current flowing through each winding of the delta connection and Line Current ( $I_L$ ) is the current flowing through each line conductor supplying the delta load. In a delta-connected system, the current relationships differ from those in a wye connection. For a balanced three-phase system, line current is equal to the phase current multiplied by  $\sqrt{3}$  in a delta connection. Mathematically,

$$I_L = \sqrt{3} * I_P$$

$$V_L = V_P$$

**Circuit diagram:**

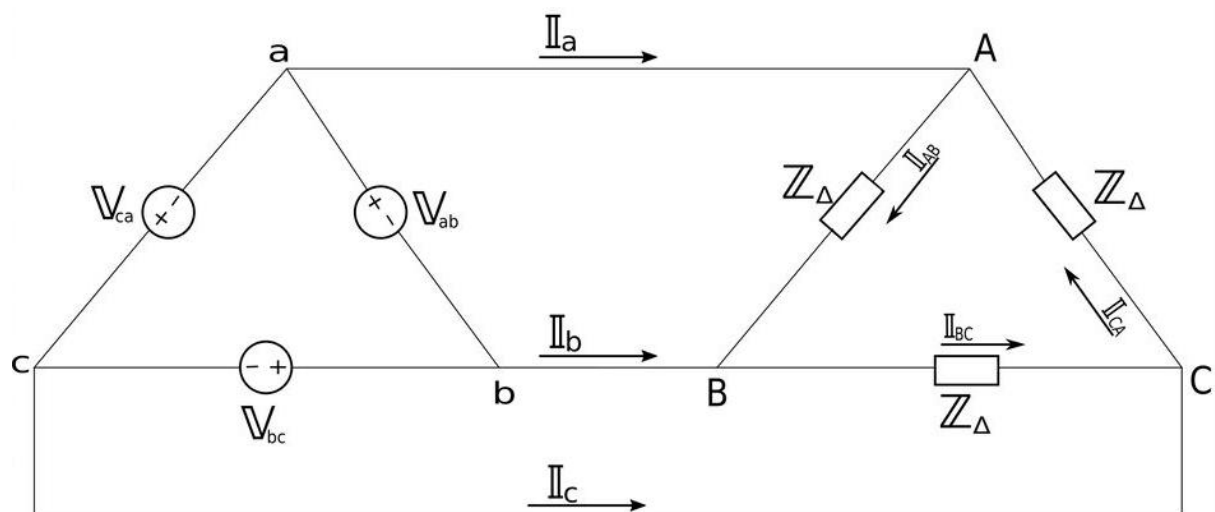


Fig:01

**Required Apparatus:**

1. Source
2. Ammeter

3. Resistor

4. Multimeter

5. Connecting Wire

**Data Table:**

S <sub>L</sub> No	I <sub>L</sub>	I <sub>P</sub> (m)	I <sub>P</sub> (c)	V <sub>P</sub>	V <sub>L</sub>	Error(%)
1	1.5	0.8	0.86	40	40	6.97
2	2.3	1.2	1.32	60	60	9.09
3	3.8	2.1	2.19	80	80	4.11
4	4.3	2.3	2.48	100	100	7.26

**Calculation:**

For the 1st one:

$$I_L = 1.5 \text{ A}, I_P(c) = I_L / \sqrt{3} = 0.86 \text{ A}, I_P(m) = 0.8 \text{ A}, \text{Error} = 6.97\%$$

For the 2nd one:

$$I_L = 2.3 \text{ A}, I_P(c) = I_L / \sqrt{3} = 1.32 \text{ A}, I_P(m) = 1.2 \text{ A}, \text{Error} = 9.09\%$$

For the 3rd one:

$$I_L = 3.8 \text{ A}, I_P(c) = I_L / \sqrt{3} = 2.19 \text{ A}, I_P(m) = 2.1 \text{ A}, \text{Error} = 4.11\%$$

For the 4th one:

$$I_L = 4.3 \text{ A}, I_P(c) = I_L / \sqrt{3} = 2.48 \text{ A}, I_P(m) = 2.3 \text{ A}, \text{Error} = 7.26\%$$

**Conclusion:**

The measured line current and phase current values were found to be consistent with theoretical calculations. The experimental results validated the theoretical relationships between line and phase currents in a delta-connected system.